

Comp E 475

Microprocessors

HW6 : PC module

Student: Giorgi Tchikoidze

Red ID #: 822089301


31.12.2019

Contents

Task Description.....	2
Solution.....	2
Simulation & Verification.....	2
Comparison.....	3
Conclusion.....	3

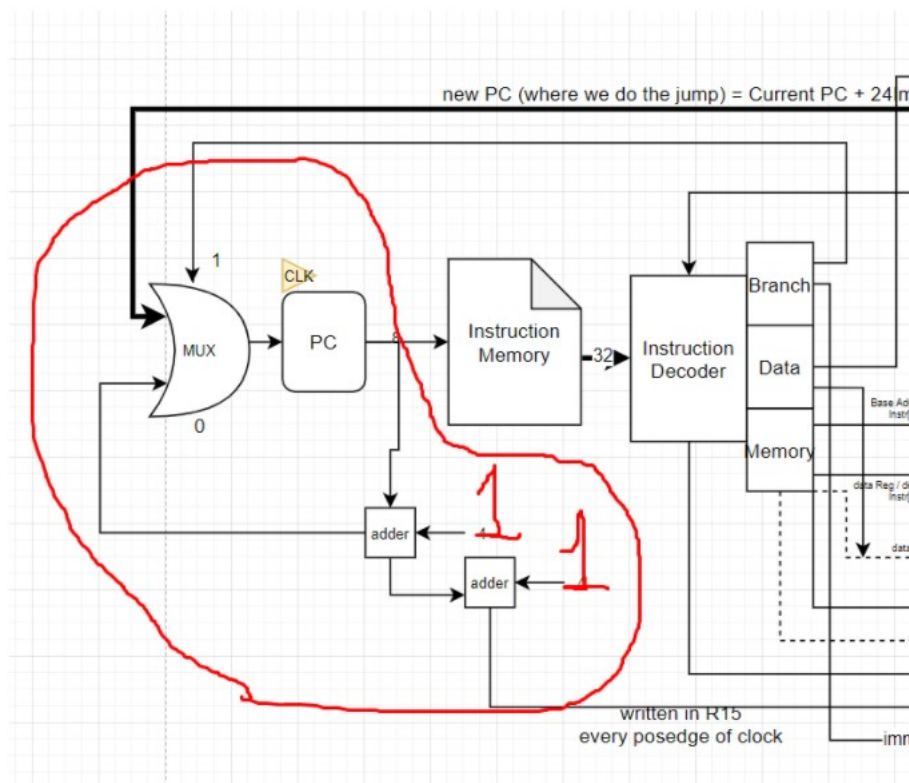Task Description

For this assignment we have to implement following controller module in verilog:



Solution

On the diagram we have two most important element: multiplexer and adder, since every output depends on them.

Multiplexer gets 3 input: select signal, jump location and incremented PC output by one. So we have to implements this according to following table:

Sel	output
0	jmp
1	pc_out+1

So we have:

```
assign mux_in = sel ? jmp : pc_out+1;
```

for adder we do not need any special solution, we can just increment registers.

Entire solution code:

```
timescale 1ns / 1ps
module pc_module(
    input clk,
    input sel,
    input [7:0] jmp,
    output reg [7:0] pc_out,
    output [7:0] r15
);
    wire [7:0] mux_in;

    always @ (posedge clk) begin
        pc_out <= mux_in;
    end

    assign mux_in = sel ? jmp : pc_out+1;
    assign r15 = pc_out + 2;
endmodule
~
~
~
```

Simulation & Verification

#Tb code:

```

module tb;
    reg clk;
    reg sel;
    reg [7:0] jmp;
    wire [7:0] pc_out;
    wire [7:0] r15;


    pc_module uut (
        .clk(clk),
        .sel(sel),
        .jmp(jmp),
        .r15(r15),
        .pc_out(pc_out)
    );

    always #10 clk <= !clk;
    always #100 sel <= !sel;
    always #100 jmp <= jmp + 10;

    initial begin
        clk = 0;
        sel = 0;
        jmp = 0;
    end
endmodule

```

#Result:

 

Conclusion

In this part, solution was very straightforward without any complicated codes.